

Microwave Transistors

Frequency (GHz)	GaAs FET		GaAs HEMT		Silicon Bipolar		GaAs HBT	
	Gain	F _{min}	Gain	F _{min}	Gain	F _{min}	Gain	F _{min}
4	20	0.5	—	—	15	2.5	—	—
8	16	0.7	—	—	9	4.5	—	—
12	12	1.0	22	0.5	6	8.0	20	4.0
18	8	1.2	16	0.9	—	—	16	—
36	—	—	12	1.7	—	—	10	—
60	—	—	8	2.6	—	—	7	—

Modeling method

• S-parameters : up to meas. freqs.


• Equivalent ckt

- freq. extrapolation


- physical

GaAs FET

Physical structure

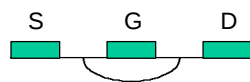

Intrinsic EC model(no pad)

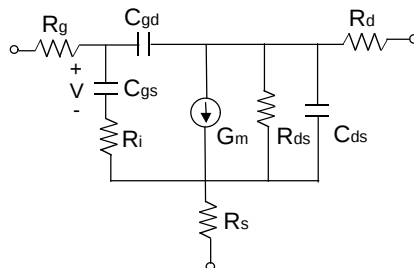


f_T (current gain cut-off freq)


$$H_{21} = \left| \frac{I_d}{I_g} \right| \approx \left| \frac{g_m V}{w C_{gs} V} \right| \approx \frac{g_m}{w C_{gs}}$$

$$f_T = \frac{g_m}{2\pi C_{gs}}$$

Biasing scheme

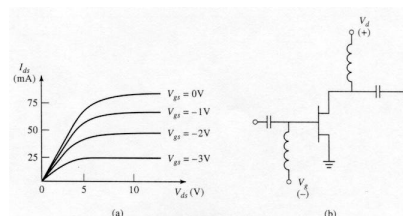

Power Gains

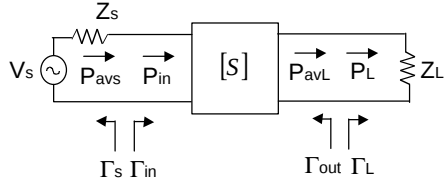

Power Gain Definition

• Power gain = G

$$G = \frac{P_L}{P_{in}} \quad : \text{indep of } Z_s$$

• Available gain = G_A

$$G_A = \frac{P_{avL}}{P_{avs}} \quad : \text{indep of } Z_L$$

• Transducer Power gain = G_T

$$G_T = \frac{P_L}{P_{avs}} \quad : \text{dep on } Z_s \text{ and } Z_L$$

Formula

$$G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{22}\Gamma_L|^2}$$

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11}\Gamma_s|^2 (1 - |\Gamma_{out}|^2)}$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_s\Gamma_{in}|^2 |1 - S_{22}\Gamma_L|^2}$$

$$G_{TU} = G_T|_{S_{12}=0} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2) (1 - |\Gamma_L|^2)}{|1 - S_{11}\Gamma_s|^2 |1 - S_{22}\Gamma_L|^2}$$

Amplifier Gain - S-parameter Approach

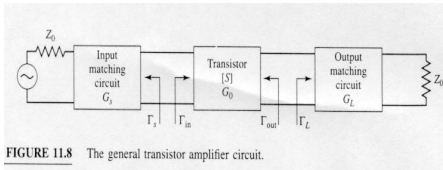


FIGURE 11.8 The general transistor amplifier circuit.

$$\bullet G_{Tot} = \frac{P_{L,S}}{P_{avs}} \cdot \frac{P_{out,D}}{P_{in,D}} \cdot \frac{P_{L,L}}{P_{in,L}}$$

$$= [G_T]_S \cdot [G]_D \cdot [G]_L$$

$$[G_T]_S = \frac{|S_{21S}|^2 (1 - |\Gamma_{in}|^2)}{|1 - S_{22S}\Gamma_{in}|^2}$$

$$[G]_D = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{22}\Gamma_L|^2}$$

$$[G]_L = \frac{|S_{21L}|^2}{1 - |\Gamma_L|^2}$$


$$G_{Tot} = \frac{|S_{21S}|^2 |S_{21}|^2 |S_{21L}|^2}{|1 - S_{22S}\Gamma_{in}|^2 |1 - S_{22}\Gamma_L|^2}$$

$$S_{22S} = \Gamma_s \rightarrow |S_{21S}|^2 = 1 - |\Gamma_s|^2$$

$$S_{11L} = \Gamma_L \rightarrow |S_{21L}|^2 = 1 - |\Gamma_L|^2$$

$$G_{Tot} = \frac{(1 - |\Gamma_s|^2) |S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - \Gamma_{in}\Gamma_s|^2 |1 - S_{22}\Gamma_L|^2}$$

Amplifier Gain - from Equivalent Circuit

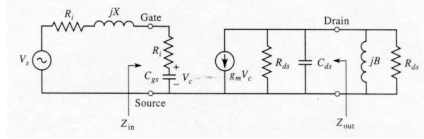

iMatching condition (Assume $C_{gd}=0 \rightarrow S_{12}=0$)

$$Z_{in} = Z_S^* \Rightarrow X = \frac{1}{\omega C_{gs}}$$

$$Z_{out} = Z_L^* \Rightarrow B = -\omega C_{ds}$$


$$\bullet G_{TU} = \frac{\frac{1}{8} |g_m V_c|^2 R_{ds}}{\frac{1}{8} |V_s|^2 / R_i} = \frac{g_m^2 R_{ds}}{4 \omega^2 R_i C_{gs}^2} = \frac{R_{ds}}{4 R_i} \left(\frac{f_T}{f} \right)^2$$

$\Rightarrow 6\text{dB/oct roll-off}$

iMaximum frequency of oscillation

$$f_{\max} = \frac{f_T}{2} \sqrt{\frac{R_{ds}}{R_{in}}} \rightarrow \text{most important parameter for Amp., Osc.}$$

Stability

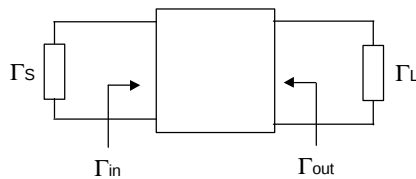

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21}}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$

$\therefore$ for some $\Gamma_S, \Gamma_L, \Gamma_{in}, \Gamma_{out}$ can be greater than 1

$\Rightarrow$ unstable!

ii Stability Circle

$|\Gamma_{in}|=1$ circle in Γ_L - plane

$\Rightarrow$ output stability circle

$|\Gamma_{out}|=1$ circle in Γ_S - plane

$\Rightarrow$ input stability circle


for $|\Gamma_{in}|=1$

$$\left| \Gamma_L - \frac{(S_{22} - \Delta S_{11})^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$\Rightarrow \text{Radius}(R_L) = \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$\text{Center}(C_L) = \frac{(S_{22} - \Delta S_{11})^*}{|S_{22}|^2 - |\Delta|^2}$$

Stability Circle

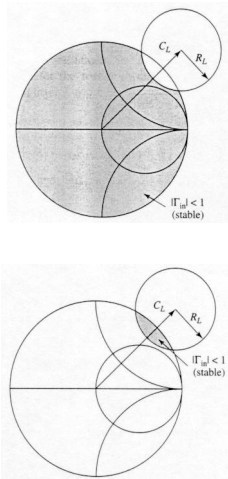

ï Stable region?(output)

i) $|S_{11}| < 1$

⇒ for $\Gamma_L = 0$, $\Gamma_{in} = S_{11} < 1$

⇒ stable for region containing $\Gamma_L = 0$

ii) $|S_{11}| > 1$

⇒ stable for region excluding $\Gamma_L = 0$

Amplifier Stability

ïStability

(1) Unconditional Stability

⇒ for all Γ_s and Γ_l

$$|\Gamma_{in}|, |\Gamma_{out}| < 1$$

(2) Conditional Stability

⇒ for some Γ_s and Γ_l

$$|\Gamma_{in}|, |\Gamma_{out}| < 1$$

ïConditions (iff)


$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|^2} > 1$$

$$\text{where } \Delta = S_{11}S_{22} - S_{12}S_{21}$$

ïConditional Stable

⇒ Need to choose Γ_s, Γ_l
for stable region

Narrowband Amplifier Design

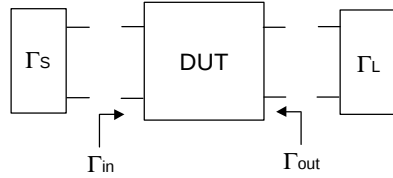

$$G_T = \frac{(1-|\Gamma_s|^2)}{|1-\Gamma_s\Gamma_{in}|^2} \cdot |S_{21}|^2 \cdot \frac{(1-|\Gamma_L|^2)}{|1-S_{22}\Gamma_L|^2}$$

$$= G_S \cdot G_0 \cdot G_L$$

$$G_S = \frac{1-|\Gamma_s|^2}{|1-\Gamma_s\Gamma_{in}|^2}$$

$$G_L = \frac{1-|\Gamma_L|^2}{|1-S_{22}\Gamma_L|^2}$$

ii Maximum gain

$$\begin{cases} \Gamma_{in} = \Gamma_s^* \\ \Gamma_{out} = \Gamma_L^* \end{cases}$$

$$G_{T_{max}} = \frac{1}{1-|\Gamma_s|^2} |S_{21}|^2 \frac{1-|\Gamma_L|^2}{|1-S_{22}\Gamma_L|^2}$$

ii Condition for simultaneous match

$$\begin{cases} \Gamma_s^* = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1-S_{22}\Gamma_L} \\ \Gamma_L^* = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1-S_{11}\Gamma_s} \end{cases}$$

$$\Rightarrow \begin{cases} \Gamma_s = \frac{B_1 \pm \sqrt{B_1^2 - 4C_1}}{2C_1} \\ \Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4C_2}}{2C_2} \end{cases}$$

where $B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$ $C_1 = S_{11} - \Delta S_{22}^*$
 $B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$ $C_2 = S_{22} - \Delta S_{11}^*$

Unilateral Case

ii Unilateral Transducer Gain

$$\Gamma_{in} = S_{11} \quad , \quad \Gamma_{out} = S_{22}$$

$$G_{TU} = \frac{|S_{21}|^2 (1-|\Gamma_s|^2) (1-|\Gamma_L|^2)}{|1-S_{11}\Gamma_s|^2 |1-S_{22}\Gamma_L|^2}$$

ii Condition for Simultaneous Match

$$\Gamma_s^* = S_{11} \quad , \quad \Gamma_L^* = S_{22}$$

ii Maximum Unilateral Gain

$$G_{TU_{max}} = \frac{1}{1-|S_{11}|^2} |S_{21}|^2 \frac{1}{1-|S_{22}|^2}$$

Mismatched Amp Design - Gain Circles(unilateral)

ï Gain for unilateral case

$$G = G_S \cdot |S_{21}|^2 \cdot G_L$$

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2}$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

ï Maximum unilateral gain

$$G_{S\max} = G_S|_{\Gamma_S=S_{11}^*} = \frac{1}{1 - |S_{11}|^2}$$

$$G_{L\max} = G_L|_{\Gamma_L=S_{22}^*} = \frac{1}{1 - |S_{22}|^2}$$

ï Gain factor g_s, g_L

$$G = G_{S\max} \cdot |S_{21}|^2 \cdot G_{L\max} \cdot \frac{G_S}{G_{S\max}} \cdot \frac{G_L}{G_{L\max}}$$

$$= G_{\max} \cdot g_s \cdot g_L$$

$$\text{where } g_s = \frac{G_S}{G_{S\max}}, \quad g_L = \frac{G_L}{G_{L\max}}$$

ï Gain circles

For given g_s , find Γ_s

$$g_s = \frac{G_S}{G_{S\max}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} (1 - |S_{11}|^2)$$


$$\Rightarrow \begin{cases} C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2} \\ R_s = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2} \end{cases}$$

⇒ Circles!

.. center : on the line to S_{11}^*


.. $\Gamma_s=0 \rightarrow G_S=1 \Rightarrow 0\text{dB}$ circle cross the center

Gain Circle and Bandwidth

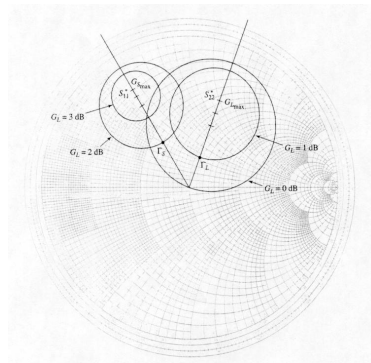


- ⇒ Choose Γ_s and Γ_L close to the center of Smith chart
- ⇒ for max bandwidth

1. Exact match design

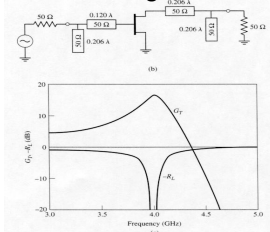

2. Mismatch design

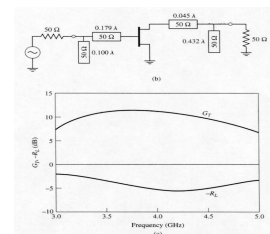

Low Noise Amplifier Design

ii Noise figure of 2-port device

$$F = F_{\min} + \frac{R_N}{G_S} |Y_S - Y_{opt}|^2$$

where $Y_S = G_S + jB_S$, $Y_{opt} = G_{opt} + jB_{opt}$

ii 4 noise parameters

.. $F_{\min}$.. R_N

.. G_{opt} .. B_{opt}

ii S-parameter representation

$$F = F_{\min} + \frac{4R_N}{Z_0} \frac{|\Gamma_S - \Gamma_{opt}|^2}{(1 - |\Gamma_S|^2)|1 + \Gamma_{opt}|^2}$$

ii Noise figure parameters

⇒ circles

$$N = \frac{F - F_{\min}}{4R_N/Z_0} |1 + \Gamma_{opt}|^2$$

⇒ determined by noise parameters


ii Constant Noise figure circles

$$N = \frac{|\Gamma_S - \Gamma_{opt}|^2}{1 - |\Gamma_S|^2}$$

$$\Rightarrow \left| \Gamma_S - \frac{\Gamma_{opt}}{N+1} \right| = \frac{\sqrt{N(N+1 - |\Gamma_{opt}|^2)}}{(N+1)}$$

* Circle center on a straight line from the center to Γ_{opt}

Low Noise Amplifier Design(cont'd)

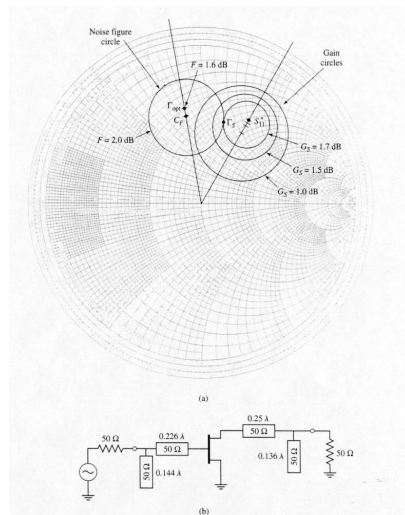

ii Amplifier design


ñ RL, Stability, Bandwidth

ii LNA design

ñ RL, Stability, NF, Bandwidth

ii Compromise between NF, RL, Stability and Gain

Oscillator - Types

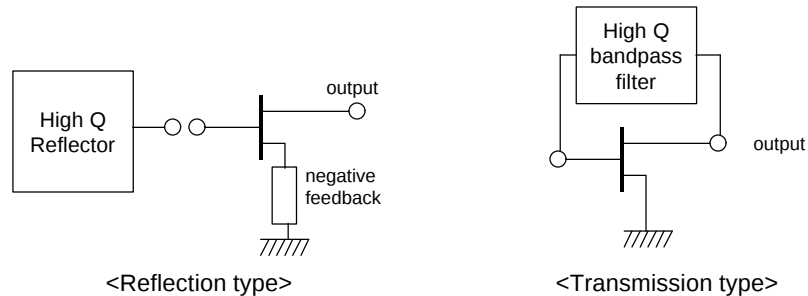


Two types of VCO

- ñ Transmission type : amplifier mode $\Rightarrow$ straightforward
- ñ Reflection type : negative resistance mode : less feed structure $\Rightarrow$ potentially higher Q factor


Y. Kwon Chap 11 : Amplifiers & Oscillators 15 Microwave Engineering Course Note, SoEE, SNU

One - port Negative Resistance Oscillator

Negative Resistance Device

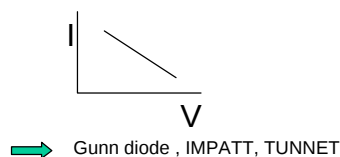

Circuit

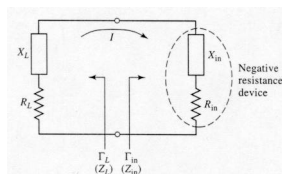

KVL

$$\rightarrow (Z_L + Z_{in})I = 0$$

$$\Rightarrow R_L + R_{in} = 0$$

$$X_L + X_{in} = 0$$

S-parameter representation

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{-Z_{in} - Z_0}{-Z_{in} + Z_0} = \frac{1}{\Gamma_L}$$

$$\Rightarrow \Gamma_L \cdot \Gamma_{in} = 1 \quad \text{at } s.s$$

Stable oscillation with perturbations in I or frequency, go back to original oscillation status


$$Z_{in}(I, \omega), Z_L(\omega)$$

$$\Rightarrow \frac{\partial(X_L + X_{in})}{\partial \omega} \gg 0$$

$\therefore$ High Q resonator needed

Y. Kwon Chap 11 : Amplifiers & Oscillators 16 Microwave Engineering Course Note, SoEE, SNU

Transistor Oscillator

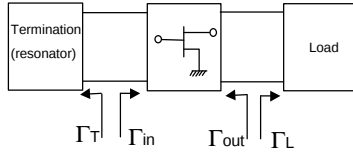

Design procedure

- Choose Γ_T for max Γ_{out} (>1)

$$Z_{out} = R_{out} + jX_{out}$$

$$\Rightarrow \text{Maximize } |R_{out}| (\text{negative})$$

- Choose $Z_L = R_L + jX_L$

$$R_L = -\frac{R_{out}}{3} \text{ (for max power)}$$

$$X_L = -X_{out}$$

Simultaneous Oscillation - output oscillator

$$\Gamma_L \cdot \Gamma_{out} = 1$$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_T}{1-S_{11}\Gamma_T} = \frac{S_{22}-\Delta\Gamma_T}{1-S_{11}\Gamma_T}$$

$$\Gamma_T = \frac{1-S_{22}\Gamma_L}{S_{11}-\Delta\Gamma_L}$$

$$\Gamma_{in} = \frac{S_{11}-\Delta\Gamma_L}{1-S_{22}\Gamma_L}$$


$$\therefore \Gamma_T \cdot \Gamma_{in} = 1$$



Input oscillation

(Large signal S-parameter)

DRO: Dielectric Resonator Oscillator

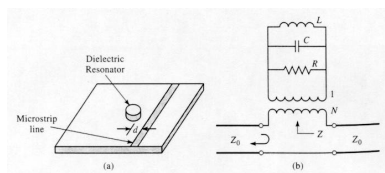

$$Z = \frac{N^2 R}{1 + j2Q\Delta w/w_0} \text{ (equivalent series impedance)}$$


- Coupling factor

$$g = \frac{Q}{Q_e} = \frac{R/w_0 L}{R_L / N^2 w_0 L} (R_L = 2Z_0)$$


- Γ at the resonator plane

$$\Gamma = \frac{(Z_0 + N^2 R) - Z_0}{Z_0 + N^2 R + Z_0} = \frac{g}{1+g}$$

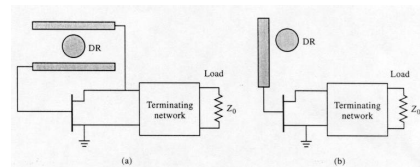$\therefore \text{Measure } \Gamma \rightarrow \text{find } g \rightarrow \text{find } N^2 R$



DRO Design

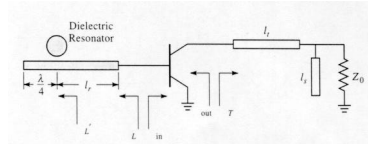

Design Procedure

Find Γ_L for max $|R_{out}|$

Design output matching circuit

$$Z_T = -\frac{R_{out}}{3} - jX_{out}$$

Transform Γ_L to Γ_L'

$$\Gamma_L' = \Gamma_L e^{j2bl_r}$$

Find Z_L'

$$Z_L' = Z_0 \frac{1 + \Gamma_L'}{1 - \Gamma_L'}$$

Find g

$$g = \frac{Z_L}{Z_0} \quad (\text{note : } Z_L = Z_0)$$

Γ_{out} vs frequency (effect of DR)

