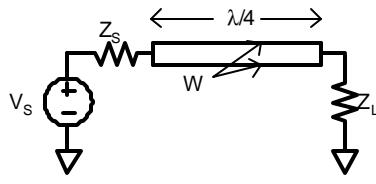




Impedance Matching with Transmission Lines



- useful functions and identities
- Units
- Constants

Table of Contents

- I. Introduction
- II. Inputs
- III. Transmission Line Synthesis Function
- IV. Single Shunt Stub Transmission Line Matching
- V. Single Series Stub Transmission Line Matching
- VI. 1/4 Wave Transformer Matching
- VII. 1/4 Wave Binomial Transformer Matching
- VIII. 1/4 Wave Chebyshev Transformer Matching
- IX. Exponential Taper Matching Transformer
- X. Triangular Taper Matching Transformer
- XI. Klopfenstein Taper Matching Transformer
- XII. Copyright and Trademark Notice

Introduction

Transmission lines have some special properties that can make them advantageous for impedance matching. First they can provide an open certain frequencies, and a short at others, making them useful for biasing, where an impedance needs to be a short at DC, but an open at a desired frequency. This property also allows them to short out harmonics of a signal, without attenuation of the desired signal. At very high frequencies (>2GHz), the physical dimensions of inductors and capacitors make them difficult to manufacture. At these frequencies, inductors and capacitors are replaced with transmission line, made cheap and small out of PC board.

Inputs

$Z_L := 100\Omega$
$Z_S := 50\Omega$
$S_{11max} := -10\text{dB}$
$f_c := 1\text{GHz}$
$\Delta f := 0.3\text{GHz}$
$\epsilon_r := 4.2$
$h := 60\text{mil}$

Load Impedance
Source Impedance
Maximum Tolerable S11
Center Frequency
Bandwidth Needed
Relative Permittivity of LTCC (Low Temperature Co-fired Ceramic)
PC Board Height for LTCC

Transmission Line Synthesis Function

$$W(\epsilon_r, h, Z_0) := \begin{cases} A \leftarrow \frac{Z_0}{60\text{ohm}} \cdot \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \cdot \left(0.23 + \frac{0.11}{\epsilon_r} \right) \\ B \leftarrow \frac{377\text{ohm} \cdot \pi}{2 \cdot Z_0 \cdot \sqrt{\epsilon_r}} \\ W_1 \leftarrow \frac{8 \cdot e^A \cdot h}{e^{2 \cdot A} - 2} \\ W_2 \leftarrow \frac{2 \cdot h}{\pi} \cdot \left[B - 1 - \ln(2 \cdot B - 1) + \frac{\epsilon_r - 1}{2 \cdot \epsilon_r} \cdot \left(\ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right) \right] \\ W \leftarrow \text{if} \left(\frac{W_1}{h} < 2, W_1, \text{if} \left(\frac{W_2}{h} > 2, W_2, 0\text{m} \right) \right) \\ W \end{cases}$$

Single Shunt Stub Transmission Line Matching

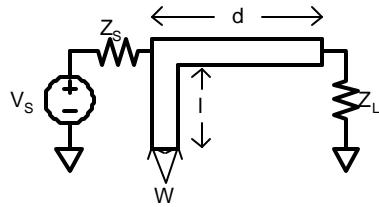


Fig. 1: Single open shunt stub matching

Here a stub and a transmission line are used to match a transmission line input, with characteristic impedance of Z_S , to a complex load of impedance Z_L . A open circuit stub, of length l , is placed at the input with a transmission line connecting it to the load with a length, d . Both transmission line segments have a characteristic impedance of Z_S . You little (choice of two implementations) control over the bandwidth for single stub tuners.

$$W_{\text{val}} := W(\epsilon_r, h, Z_S)$$

$$W_{\text{val}} = 3.016 \text{ mm}$$

Width of Transmission Lines

$$\omega_c := 2 \cdot \pi \cdot f_c$$

$$\omega_c = 6.283 \times 10^9 \frac{\text{rad}}{\text{sec}}$$

Center Frequency

$$\lambda := \frac{2 \cdot \pi \cdot c}{\omega_c}$$

$$\lambda = 29.9 \text{ cm}$$

Wavelength in Free Space

$$R_L := \text{Re}(Z_L)$$

$$R_L = 100 \Omega$$

Real Part of Load Impedance

$$X_L := \text{Im}(Z_L)$$

$$X_L = 0 \Omega$$

Imag part of Load Impedance

When designing transmission line transformers, there are multiple solutions to the matching problem. For an example, an additional wavelength of transmission line can be added to yield the same matching, but with a different frequency response. This is usually not done to keep the area small. Here multiple solutions are presented.

$$t_1 := \frac{X_L + \sqrt{\frac{R_L}{Z_S} \cdot [(Z_S - R_L)^2 + X_L^2]}}{R_L - Z_S}$$

$$t_1 = 1.414$$

Coefficient for First Solution

$$t_2 := \frac{X_L - \sqrt{\frac{R_L}{Z_S} \cdot [(Z_S - R_L)^2 + X_L^2]}}{R_L - Z_S}$$

$$t_2 = -1.414$$

Coefficient for Second Solution

$$d_1 := \lambda \cdot \frac{1}{2\pi} \cdot \text{atan}(t_1)$$

$$d_1 = 4.546 \text{ cm}$$

$$d_2 := \lambda \cdot \frac{1}{2\pi} \cdot (\pi + \text{atan}(t_2))$$

$$d_2 = 10.404 \text{ cm}$$

$$B_{s1} := -\frac{R_L^2 \cdot t_1 - (Z_S - X_L \cdot t_1) \cdot (X_L + Z_S \cdot t_1)}{Z_S \left[R_L^2 + (X_L + Z_S \cdot t_1)^2 \right]}$$

$$\frac{1}{B_{s1}} = -70.711 \text{ ohm}$$

$$B_{s2} := -\frac{R_L^2 \cdot t_2 - (Z_S - X_L \cdot t_2) \cdot (X_L + Z_S \cdot t_2)}{Z_S \left[R_L^2 + (X_L + Z_S \cdot t_2)^2 \right]}$$

$$\frac{1}{B_{s2}} = 70.711 \text{ ohm}$$

$$l_{o1} := \frac{\lambda}{2\pi} \cdot \text{atan}(B_{s1} \cdot Z_S)$$

$$l_{o1} = -29.289 \text{ mm}$$

$$l_{s1} := \frac{-\lambda}{2\pi} \cdot \text{atan}\left(\frac{1}{B_{s1} \cdot Z_S}\right)$$

$$l_{s1} = 45.461 \text{ mm}$$

$$l_{o2} := \frac{\lambda}{2\pi} \cdot \text{atan}(B_{s2} \cdot Z_S)$$

$$l_{o2} = 29.289 \text{ mm}$$

$$l_{s2} := \frac{-\lambda}{2\pi} \cdot \text{atan}\left(\frac{1}{B_{s2} \cdot Z_S}\right)$$

$$l_{s2} = -45.461 \text{ mm}$$

Some solutions are not valid (negative lengths), so they are dropped:

$$OK_1 := (l_{o1} > 0) \cdot (d_1 > 0)$$

$$OK_1 = 0$$

$$OK_2 := (l_{o2} > 0) \cdot (d_2 > 0)$$

$$OK_2 = 1$$

$$OK_3 := (l_{s1} > 0) \cdot (d_1 > 0)$$

$$OK_3 = 1$$

$$OK_4 := (l_{s2} > 0) \cdot (d_2 > 0)$$

$$OK_4 = 0$$

$$Area_1 := (l_{o1} + d_1) \cdot W_{val}$$

$$Area_1 = 0.488 \text{ cm}^2$$

$$Area_2 := (l_{o2} + d_2) \cdot W_{val}$$

$$Area_2 = 4.021 \text{ cm}^2$$

$$Area_3 := (l_{s1} + d_1) \cdot W_{val}$$

$$Area_3 = 2.742 \text{ cm}^2$$

$$Area_4 := (l_{s2} + d_2) \cdot W_{val}$$

$$Area_4 = 1.767 \text{ cm}^2$$

$$l_{o1} \cdot d_1 = -13.315 \text{ cm}^2$$

$$l_{o2} \cdot d_2 = 30.472 \text{ cm}^2$$

$$l_{s1} \cdot d_1 = 20.667 \text{ cm}^2$$

$$l_{s2} \cdot d_2 = -47.297 \text{ cm}^2$$

**Connecting Transmission L
(Solution #1&3)**

**Connecting Transmission L
(Solution #2&4)**

Susceptance of Stub (Solution #1&

Susceptance of Stub (Solution #2&

**Length of Open Circuit Stuk
(Solution #1)**

**Length of Short Circuit Stuk
(Solution #3)**

**Length of Open Circuit Stuk
(Solution #2)**

**Length of Short Circuit Stuk
(Solution #4)**

Is Solution #1 OK to use?

Is Solution #2 OK to use?

Is Solution #3 OK to use?

Is Solution #4 OK to use?

Area for Solution #1

Area for Solution #2

Area for Solution #1

Area for Solution #2

Areas if white space is considered

Single Series Stub Transmission Line Matching

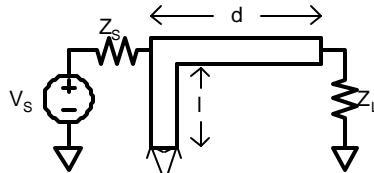


Fig. 1: Single series stub matching

$$G_L := \operatorname{Re}\left(\frac{1}{Z_L}\right) \quad B_L := \operatorname{Im}\left(\frac{1}{Z_L}\right)$$

$$Y_S := \frac{1}{Z_S}$$

$$t_1 := \frac{B_L + \sqrt{\frac{G_L}{Y_S} \cdot [(Y_S - G_L)^2 + B_L^2]}}{G_L - Y_S}$$

$$t_2 := \frac{B_L - \sqrt{\frac{G_L}{Y_S} \cdot [(Y_S - G_L)^2 + B_L^2]}}{G_L - Y_S}$$

$$d_1 := \lambda \cdot \frac{1}{2\pi} \cdot \operatorname{atan}(t_1)$$

$$d_2 := \lambda \cdot \frac{1}{2\pi} \cdot (\pi + \operatorname{atan}(t_2))$$

$$X_{S1} := \frac{G_L^2 \cdot t_1 - (Y_S - t_1 \cdot B_L) \cdot (B_L + t_1 \cdot Y_S)}{-Y_S [G_L^2 + (B_L + t_1 \cdot Y_S)^2]}$$

$$X_{S2} := \frac{G_L^2 \cdot t_2 - (Y_S - t_2 \cdot B_L) \cdot (B_L + t_2 \cdot Y_S)}{-Y_S [G_L^2 + (B_L + t_2 \cdot Y_S)^2]}$$

$$l_{o1} := \frac{-\lambda}{2\pi} \cdot \operatorname{atan}\left(\frac{Z_S}{X_{S1}}\right)$$

$$l_{s1} := \frac{\lambda}{2\pi} \cdot \operatorname{atan}\left(\frac{X_{S1}}{Z_S}\right)$$

$$l_{o2} := \frac{-\lambda}{2\pi} \cdot \operatorname{atan}\left(\frac{Z_S}{X_{S2}}\right)$$

$$l_{s2} := \frac{\lambda}{2\pi} \cdot \operatorname{atan}\left(\frac{X_{S2}}{Z_S}\right)$$

$$\text{OK}_1 := (l_{o1} > 0) \cdot (d_1 > 0)$$

$$\text{OK}_2 := (l_{o2} > 0) \cdot (d_2 > 0)$$

$$\text{OK}_3 := (l_{s1} > 0) \cdot (d_1 > 0)$$


$$\text{OK}_4 := (l_{s2} > 0) \cdot (d_2 > 0)$$

$$\text{Area}_1 := (l_{o1} + d_1) \cdot W_{val}$$

$$\text{Area}_2 := (l_{o2} + d_2) \cdot W_{val}$$

$$\text{Area}_3 := (l_{s1} + d_1) \cdot W_{val}$$
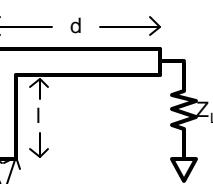
$$\text{Area}_4 := (l_{s2} + d_2) \cdot W_{val}$$



Load Conductance and Suseptance

Source Admittance

Coefficient for First Solution

$$d_1 = -2.929 \text{ cm}$$

Connecting Transmission Line
(Solution #1&3)

$$d_2 = 17.879 \text{ cm}$$

Connecting Transmission Line
(Solution #2&4)

$$X_{S1} = -35.355 \Omega \text{ Stub Reactance (Solution #1)}$$

$$X_{S2} = 35.355 \Omega \text{ Stub Reactance (Solution #2)}$$

$$l_{o1} = 45.461 \text{ mm}$$

Length of Open Circuit Stub
(Solution #1)

$$l_{s1} = -29.289 \text{ mm}$$

Length of Short Circuit Stub
(Solution #3)

$$l_{o2} = -45.461 \text{ mm}$$

Length of Open Circuit Stub
(Solution #2)

$$l_{s2} = 29.289 \text{ mm}$$

Length of Short Circuit Stub
(Solution #4)

Is Solution #1 OK to use?

$$\text{OK}_1 = 0$$

Is Solution #2 OK to use?

$$\text{OK}_2 = 0$$

Is Solution #3 OK to use?

$$\text{OK}_3 = 0$$

Is Solution #4 OK to use?

$$\text{OK}_4 = 1$$

$$\text{Area}_1 = 0.488 \text{ cm}^2$$

Area for Solution #1

$$\text{Area}_2 = 4.021 \text{ cm}^2$$

Area for Solution #2

$$\text{Area}_3 = -1.767 \text{ cm}^2$$

Area for Solution #1

$$\text{Area}_4 = 6.276 \text{ cm}^2$$

Area for Solution #2

1/4 Wave Transformer Matching

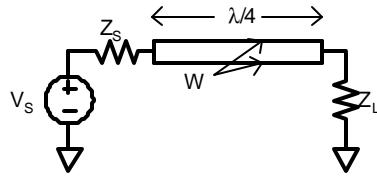


Fig. 1: Single shunt stub matching

No control over bandwidth achieved

$$\Delta f/f_c := \frac{\Delta f}{f_c}$$

$$\Gamma_{\max} := 10^{-\frac{S_{11\max}}{10}}$$

$$Z_{1_4} := \sqrt{Z_S \cdot Z_L}$$

$$\Delta f/f_{c\max} := 2 - \frac{4}{\pi} \cdot \text{acos} \left(\frac{\Gamma_{\max}}{\sqrt{1 - \Gamma_{\max}^2}} \cdot \frac{2 \cdot \sqrt{Z_S \cdot Z_L}}{|Z_L - Z_S|} \right)$$

$$OK := \Delta f/f_{c\max} > \Delta f/f_c$$

$$\beta := \frac{2 \cdot \pi}{\lambda} \cdot \sqrt{\epsilon_r}$$

$$\text{len} := \frac{\lambda}{4}$$

$$W_{\text{val}} := W(\epsilon_r, h, Z_{1_4})$$

$$\text{Area} := \text{len} \cdot W_{\text{val}}$$

Outputs

Z_{1_4} = 70.711 Ω

OK = 1

Area = 1.203 cm²

$\Delta f/f_c = 30\%$

Fractional Bandwidth Needed

$\Gamma_{\max} = 0.1$

Reflection Coefficient Needed

$Z_{1_4} = 70.711 \Omega$

Impedance of Quarter Wave Transn

$\Delta f/f_{c\max} = 36.7\%$

OK to use this circuit?

$\beta = 43.066 \text{ m}^{-1}$

Phase Constant (Wave Number)

$\text{len} = 7.475 \text{ cm}$

Length of Transformer

$W_{\text{val}} = 1.61 \text{ mm}$

Width of Transformer

$\text{Area} = 1.203 \text{ cm}^2$

Area of Transformer

Impedance of Line

OK to use this circuit?

Area of Transformer

1/4 Wave Binomial Transformer Matching

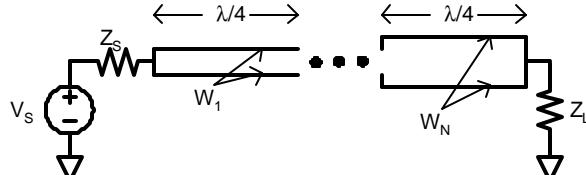


Fig. 1: 1/4 wave binomial transformer matching

$$\Gamma_{DC} := \frac{Z_L - Z_S}{Z_L + Z_S}$$

$$\Gamma_{DC} = 0.333$$

DC Reflection Coefficient

$$\frac{\ln\left(\frac{\Gamma_{max}}{|\Gamma_{DC}|}\right)}{\ln\left[\cos\left[\frac{\pi}{2}\left(1 - \frac{\Delta f_f_c}{2}\right)\right]\right]} = 0.828$$

Fractional Order Needed

$$N := \text{ceil}\left[\frac{\ln\left(\frac{\Gamma_{max}}{|\Gamma_{DC}|}\right)}{\ln\left[\cos\left[\frac{\pi}{2}\left(1 - \frac{\Delta f_f_c}{2}\right)\right]\right]}\right]$$

$$N = 1$$

Order Estimation

$$A(N) := 2^{-N} \cdot \Gamma_{DC}$$


$$A(N) = 0.167$$

Binomial Coefficient

$$\Delta f_f_c(N) := 2 - \frac{4}{\pi} \cdot \arccos\left[\frac{1}{2} \cdot \left(\frac{\Gamma_{max}}{|A(N)|}\right)^{\frac{1}{N}}\right]$$

$$\Delta f_f_c(N) = 38.795 \%$$

Actual Fractional Bandwidth

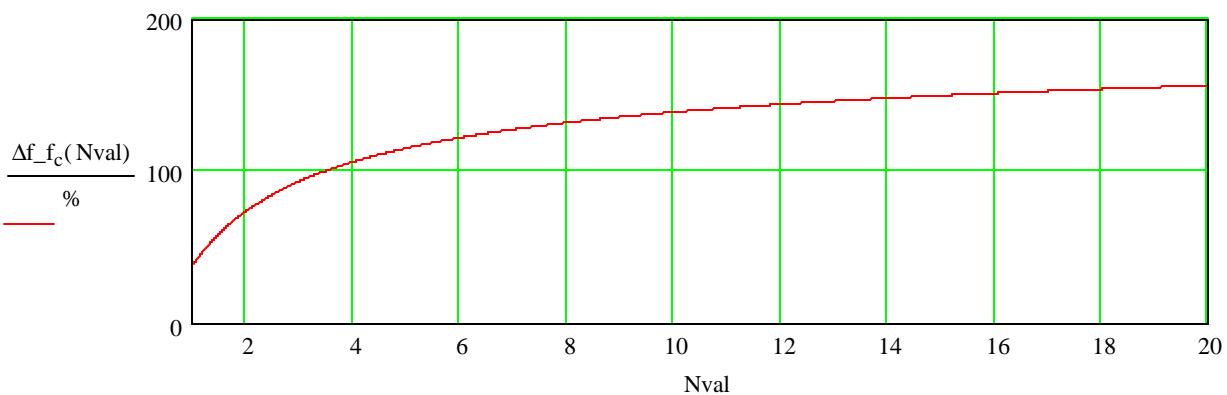

$$i := 0..(N - 1)$$

Index Vector

$$C(n, N) := \frac{N!}{(N - n)! \cdot n!}$$

Binomial Coefficients

$$C(i, N) =$$

1

$$\Gamma(n, N) := A(N) \cdot C(n, N)$$

Reflection Coefficients

$$\boxed{0.167}$$

j := 1.. N

$$Z := \begin{cases} Z_{val_0} \leftarrow Z_S \\ \text{for } i \in 0..(N-1) \\ \quad Z_{val_{i+1}} \leftarrow Z_{val_i} \cdot \left(\frac{\Gamma(i, N) + 1}{1 - \Gamma(i, N)} \right) \\ Z_{val} \end{cases}$$

$$W_{val_j} := W(\epsilon_r, h, Z_j)$$

$$\max(W_{val}) = 1.643 \text{ mm}$$

$$len := \frac{\lambda}{4} \cdot N$$

$$Area := len \cdot \max(W_{val})$$

Outputs

$$W_{val} = \begin{pmatrix} 0 \\ 1.643 \end{pmatrix} \text{ mm}$$

$$len = 7.475 \text{ cm}$$

$$Area = 1.228 \text{ cm}^2$$

$$Z_j = \\ \boxed{70} \quad \Omega$$

T-Line Impedances

$$W_{val} = \begin{pmatrix} 0 \\ 1.643 \end{pmatrix} \text{ mm}$$

Widths of Transmission Line Segments

Maximum Width

$$len = 7.475 \text{ cm}$$

Length of Transformer

$$Area = 1.228 \text{ cm}^2$$

Area of Transformer

Widths of Line Segments

Length of Transformer

Area of Transformer

1/4 Wave Chebyshev Transformer Matching

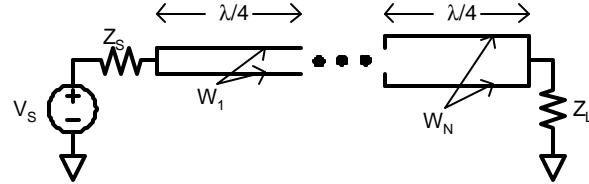



Fig. 1: 1/4 wave chebyshev transformer matching

$$\frac{\operatorname{acosh}\left(\frac{|\Gamma_{DC}|}{\Gamma_{max}}\right)}{\operatorname{acosh}\left[\sec\left(\frac{\pi}{2} \cdot \left(1 - \frac{\Delta f}{2 \cdot f_c}\right)\right)\right]} = 0.878 \quad \text{Fractional Order Needed}$$

$$N := \operatorname{ceil}\left[\frac{\operatorname{acosh}\left(\frac{|\Gamma_{DC}|}{\Gamma_{max}}\right)}{\operatorname{acosh}\left[\sec\left(\frac{\pi}{2} \cdot \left(1 - \frac{\Delta f}{2 \cdot f_c}\right)\right)\right]}\right] \quad N = 1 \quad \text{Order Estimation}$$

$$N := \operatorname{if}(N > 2, N, 2) \quad N = 2$$

$$\Delta f \cdot f_c(N) := 2 - \frac{4}{\pi} \cdot \operatorname{asec}\left(\cosh\left(\frac{1}{N} \cdot \operatorname{acosh}\left(\frac{|\Gamma_{DC}|}{\Gamma_{max}}\right)\right)\right) \quad \Delta f \cdot f_c(N) = 95.098 \% \quad \text{Actual Fractional Bandwidth}$$

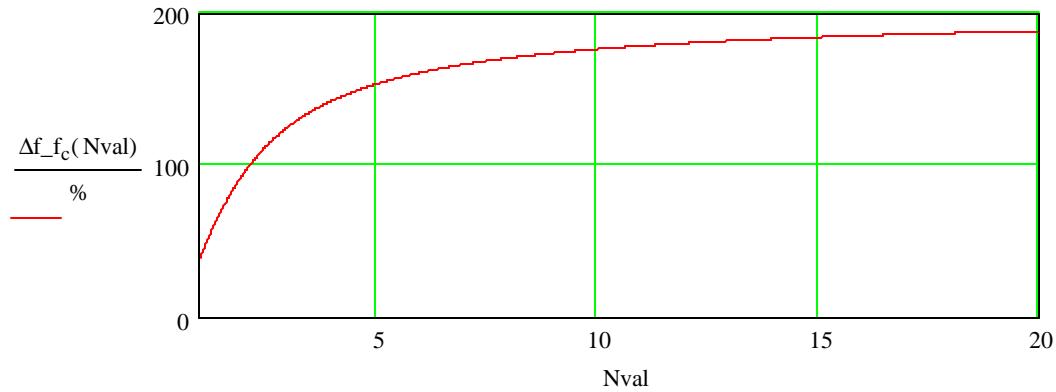

$$A := \Gamma_{max} \quad A = 0.1 \quad \text{Transformer Coefficient}$$

$$\theta_{max} := \operatorname{asec}\left(\cosh\left(\frac{1}{N} \cdot \operatorname{acosh}\left(\frac{\ln\left(\frac{Z_L}{Z_S}\right)}{2 \cdot \Gamma_{max}}\right)\right)\right) \quad \theta_{max} = 47.993 \text{ deg}$$

$T(n, x) := \text{if}(|x| < 1, \cos(n \cdot \arccos(x)), \cosh(n \cdot \text{acosh}(x)))$
 $i := 0.. N$

$$\Gamma(n) := \begin{cases} \frac{A}{2} \cdot \sec(\theta_{\max})^3 & \text{if } n = 0 \\ \frac{3}{2} \cdot A \cdot \left(\sec(\theta_{\max})^3 - \sec(\theta_{\max}) \right) & \text{if } n = 1 \\ \frac{3}{2} \cdot A \cdot \left(\sec(\theta_{\max})^3 - \sec(\theta_{\max}) \right) & \text{if } n = 2 \\ \frac{A}{2} \cdot \sec(\theta_{\max})^3 & \text{if } n = 3 \end{cases}$$

$\Gamma(i) =$

0.167
0.276
0.276

$j := 1.. N$

$$Z := \begin{cases} Z_{val_0} \leftarrow Z_S \\ \text{for } i \in 0.. N - 1 \\ Z_{val_{i+1}} \leftarrow Z_{val_i} \cdot e^{2 \cdot \Gamma(i)} \\ Z_{val} \end{cases}$$

$$W_{val_j} := W(\epsilon_r, h, Z_j)$$

$$\max(W_{val}) = 1.652 \text{ mm}$$

$$\text{len} := \frac{\lambda}{4} \cdot N$$

$$\text{Area} := \text{len} \cdot \max(W_{val})$$

Outputs

$$W_{val} = \begin{pmatrix} 0 \\ 1.652 \\ 0.401 \end{pmatrix} \text{ mm}$$

$$\text{len} = 14.95 \text{ cm}$$

$$\text{Area} = 2.47 \text{ cm}^2$$

Chebyshev Polynomial Coefficients
Index Vector

Reflection Coefficients

$$Z_j = \begin{cases} 69.803 \\ 121.31 \end{cases} \Omega$$

$$W_{val} = \begin{pmatrix} 0 \\ 1.652 \\ 0.401 \end{pmatrix} \text{ mm}$$

Maximum Width

$$\text{len} = 14.95 \text{ cm}$$

$$\text{Area} = 2.47 \text{ cm}^2$$

Widths of Transmission Line Segments
Length of Transformer
Area of Transformer

Exponential Taper Matching Transformer

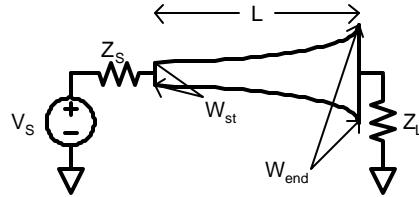


Fig. 1: Exponential transformer matching

$$L := \frac{\pi}{\beta}$$

$$L_2 := \frac{2 \cdot \pi}{\beta}$$

$$Z(z) := Z_S \cdot e^{\frac{1}{L} \cdot \ln\left(\frac{Z_L}{Z_S}\right) \cdot z}$$



$$L = 7.295 \text{ cm}$$

Length of Transformer (Option #1: $\beta L = \pi$)

$$L_2 = 14.59 \text{ cm}$$

Length of Transformer (Option #2: $\beta L = 2\pi$)
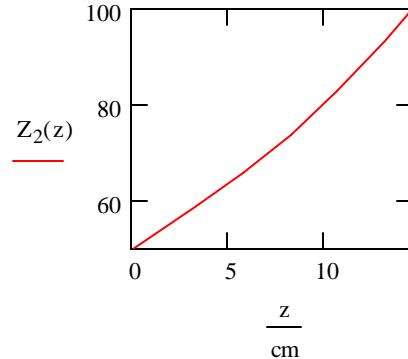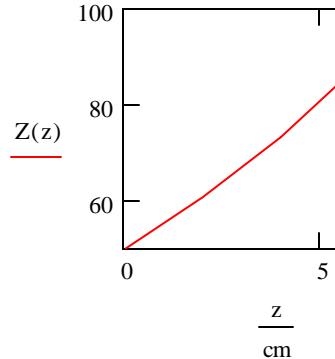
$$Z_2(z) := Z_S \cdot e^{\frac{1}{L_2} \cdot \ln\left(\frac{Z_L}{Z_S}\right) \cdot z}$$



$$W(\epsilon_r, h, Z(0\text{cm})) = 3.016 \text{ mm}$$

$$W(\epsilon_r, h, Z(L)) = 0.714 \text{ mm}$$

$$\text{TotArea} := L \cdot W(\epsilon_r, h, Z(0\text{cm}))$$

Width at Beginning of Taper

Width at End of Taper

Total Area of Transformer

$$\text{TotArea} = 2.2 \text{ cm}^2$$

Triangular Taper Matching Transformer

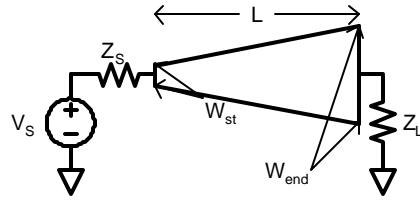



Fig. 1: Triangular transformer matching

$$L := \frac{2 \cdot \pi}{\beta}$$

$$L = 14.59 \text{ cm}$$

Length of Transformer (Option #1)
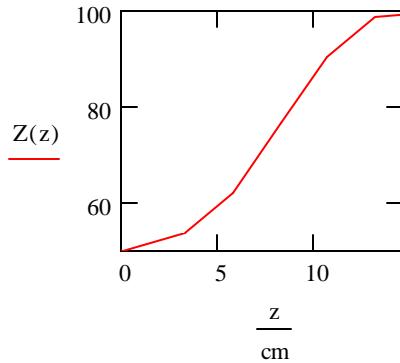
$$Z(z) := \text{if} \left[z < \frac{L}{2}, Z_S \cdot e^{2 \cdot \left(\frac{z}{L} \right)^2 \cdot \ln \left(\frac{Z_L}{Z_S} \right)}, Z_S \cdot e^{\left[4 \cdot \frac{z}{L} - 2 \cdot \left(\frac{z}{L} \right)^2 - 1 \right] \cdot \ln \left(\frac{Z_L}{Z_S} \right)} \right]$$



$$W(\epsilon_r, h, Z(0\text{cm})) = 3.016 \text{ mm}$$

$$W(\epsilon_r, h, Z(L)) = 0.714 \text{ mm}$$

$$\text{TotArea} := L \cdot W(\epsilon_r, h, Z(0\text{cm}))$$

$$\text{TotArea} = 4.401 \text{ cm}^2$$

Width at Beginning of Taper

Width at End of Taper

Total Area of Transformer

Klopfenstein Taper Matching Transformer

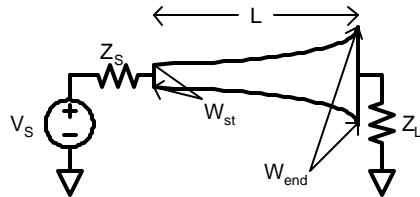


Fig. 1: Klopfenstein transformer matching

$$A := \operatorname{acosh} \left(\frac{\Gamma_{DC}}{\Gamma_{max}} \right)$$

$$L := \frac{A}{\beta}$$

$$A = 1.874$$

Coefficient for Transformer

$$L = 4.351 \text{ cm}$$



Length of Transformer

$$\phi(x, A) := \int_0^x \frac{Ii(A \cdot \sqrt{1 - y^2})}{A \cdot \sqrt{1 - y^2}} dy$$

$$Z(z) := Z_S e^{-\frac{1}{2} \cdot \ln \left(\frac{Z_L}{Z_S} \right) + \frac{\Gamma_{DC}}{\cosh(A)} \cdot A^2 \cdot \phi \left(\frac{2 \cdot z}{L} - 1, A \right)}$$

$$Z(0\text{cm}) = 55.995 \Omega \quad Z(L) = 89.294 \Omega$$
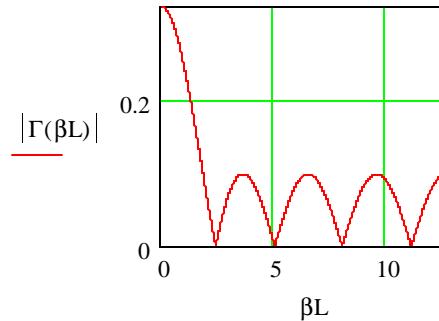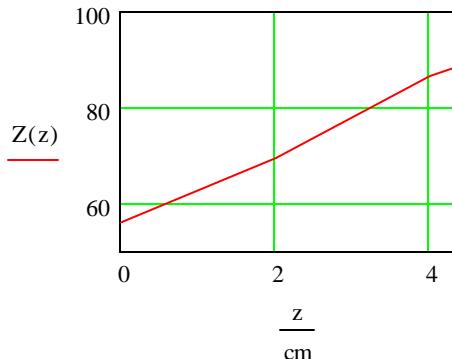
$$\Gamma(\beta L) := \Gamma_{DC} \cdot e^{-\sqrt{-1} \cdot \beta L} \cdot \frac{\cos(\sqrt{\beta L^2 - A^2})}{\cosh(A)}$$



$$W(\epsilon_r, h, Z(0\text{cm})) = 2.492 \text{ mm}$$

$$W(\epsilon_r, h, Z(L)) = 0.956 \text{ mm}$$

$$\text{TotArea} := L \cdot W(\epsilon_r, h, Z(0\text{cm}))$$

Width at Beginning of Taper

Width at End of Taper

Total Area of Transformer

$$\text{TotArea} = 1.084 \text{ cm}^2$$

Copyright and Trademark Notice

All software and other materials included in this document are protected by copyright, and are owned or controlled by Circuit Sage.

The routines are protected by copyright as a collective work and/or compilation, pursuant to federal copyright laws, international conventions, and other copyright laws. Any reproduction, modification, publication, transmission, transfer, sale, distribution, performance, display or exploitation of any of the routines, whether in whole or in part, without the express written permission of Circuit Sage is prohibited.